

# BUILD THIS

## SPEECH SYNTHESIZER

*Build this five-IC speech synthesizer and let your fingers do the talking.*

L. STEVEN CHEAIRS

WHETHER THEY'RE USED FOR INSTRUMENTATION or for practical applications, many electronic devices provide us with visual readouts. Those can range from simple indicator lights to complex LED or LCD arrays, up to and including alphanumeric displays.

Frequently, though, it would be useful to have the information without having to look at the device. There are already DMM's that provide an audible continuity-test function using a tone, but wouldn't it be convenient if the meter could tell you what voltage was being measured so you wouldn't have to take your eyes off your work? Or, how about your own talking clock—one that *really* "tells time?"

What's required for devices of that sort is speech synthesis. And while speech synthesizers have been with us for a while, it is only recently that they have been reduced to a couple of IC's and their cost come down to a reason-

able level. One such speech-synthesis system is the *Digitalker* from National Semiconductor.

### About the circuit

The *Digitalker* system consists of three N-channel MOS integrated circuits. The main IC is referred to as the Speech-Processor Chip, or SPC; its pin-out is shown in Fig. 1. The other two IC's (see Fig. 2) are ROM's containing the speech data that is processed by the SPC to produce words or phrases. Add a power supply, clock network, filter, and an audio amplifier to the *Digitalker* IC's and you will have a system that produces high-quality speech. That synthesized (actually, reconstructed) speech has the natural inflection and emphasis of the original speech. Male, female, and children's voices can be reproduced easily. (Some other speech-synthesis systems have had difficulties in reproducing the higher frequencies

required for other than male voices.)

The *Digitalker's* ROM's store only those speech elements that the ear needs to hear. (The vocal tract also generates sounds that do not convey any intelligible information.) The techniques used by National to process a speech waveform are broken into two basic categories: digitization and compression.

Recordings of actual speech are sampled for digitization (turning analog values into binary numbers) at a rate at least twice that of the highest frequency in the waveform's pattern. If the highest frequency to be used were 3000 Hz, the sampling frequency would have to be at least 6000 Hz. That sampling frequency is called the Nyquist rate.

To minimize the storage space needed for the speech information, Dr. Forrest S. Mozer developed four compression schemes. The first removes all redundant (unnecessarily repeated) pitch

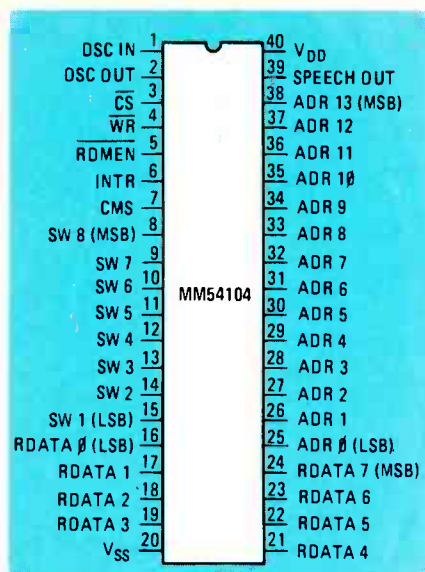


FIG. 1—THE HEART OF THE SPEECH synthesizer is National Semiconductor's MM54104.

periods and portions of certain other pitch periods. Redundant phonemes (individual sounds that, when strung together, make up speech) are also removed at this stage.

The second stage of compression, adaptive delta-modulation, involves storing the arithmetic differences of successive wave-amplitudes. By using that technique, rather than storing the amplitude values themselves, storage requirements are further minimized.

The third compression technique removes the direction component of the speech waveform. That is done by a process called phase-angle adjustment. The ear doesn't use that component, so its removal will not affect speech quality.

The last compression technique allows the amount of ROM required to store the speech data to be reduced by 50%. It does that by reducing the low-

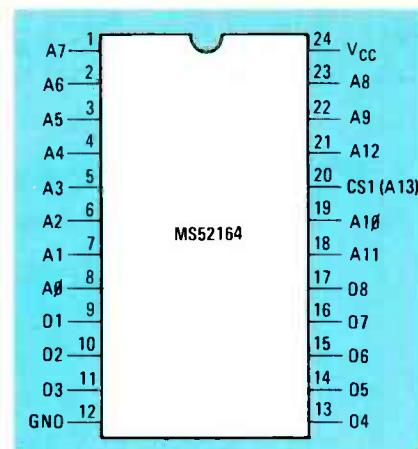


FIG. 2—THE MS52164 is a 8192 × 8 ROM used to contain speech data.

amplitude portion of a waveform to silence.

The result of using multiple compres-

TABLE 1

Word	8-bit binary address			8-bit binary address			8-bit binary address		
	S8	S1		S8	S1		S8	S1	
THIS IS DIGITALKER	00000000	Q		00110000	IS		01100000		
ONE	00000001	R		00110001	IT		01100001		
TWO	00000010	S		00110010	KILO		01100010		
THREE	00000011	T		00110011	LEFT		01100011		
FOUR	00000100	U		00110100	LESS		01100100		
FIVE	00000101	V		00110101	LESSER		01100101		
SIX	00000110	W		00110110	LIMIT		01100110		
SEVEN	00000111	X		00110111	LOW		01100111		
EIGHT	00001000	Y		00111000	LOWER		01101000		
NINE	00001001	Z		00111001	MARK		01101001		
TEN	00001010	AGAIN		00111010	METER		01101010		
ELEVEN	00001011	AMPERE		00111011	MILE		01101011		
TWELVE	00001100	AND		00111100	MILLI		01101100		
THIRTEEN	00001101	AT		00111101	MINUS		01101101		
FOURTEEN	00001110	CANCEL		00111110	MINUTE		01101110		
FIFTEEN	00001111	CASE		00111111	NEAR		01101111		
SIXTEEN	00010000	CENT		01000000	NUMBER		01110000		
SEVENTEEN	00010001	400HERTZ TONE		01000001	OF		01110001		
EIGHTEEN	00010010	80HERTZ TONE		01000010	OFF		01110010		
NINETEEN	00010011	20MS SILENCE		01000011	ON		01110011		
TWENTY	00010100	40MS SILENCE		01000100	OUT		01110100		
THIRTY	00010101	80MS SILENCE		01000101	OVER		01110101		
FORTY	00010110	160MS SILENCE		01000110	PARENTHESIS		01110110		
FIFTY	00010111	320MS SILENCE		01000111	PERCENT		01110111		
SIXTY	00011000	CENTI		01001000	PLEASE		01111000		
SEVENTY	00011001	CHECK		01001001	PLUS		01111001		
EIGHTY	00011010	COMMA		01001010	POINT		01111010		
NINETY	00011011	CONTROL		01001011	POUND		01111011		
HUNDRED	00011100	DANGER		01001100	PULSES		01111100		
THOUSAND	00011101	DEGREE		01001101	RATE		01111101		
MILLION	00011110	DOLLAR		01001110	RE		01111110		
ZERO	00011111	DOWN		01001111	READY		01111111		
A	00100000	EQUAL		01010000	RIGHT		10000000		
B	00100001	ERROR		01010001	SS		10000001		
C	00100010	FEET		01010010	SECOND		10000010		
D	00100011	FLOW		01010011	SET		10000011		
E	00100100	FUEL		01010100	SPACE		10000100		
F	00100101	GALLON		01010101	SPEED		10000101		
G	00100110	GO		01010110	STAR		10000110		
H	00100111	GRAM		01010111	START		10000111		
I	00101000	GREAT		01011000	STOP		10001000		
J	00101001	GREATER		01011001	THAN		10001001		
K	00101010	HAVE		01011010	THE		10001010		
L	00101011	HIGH		01011011	TIME		10001011		
M	00101100	HIGHER		01011100	TRY		10001100		
N	00101101	HOUR		01011101	UP		10001101		
O	00101110	IN		01011110	VOLT		10001110		
P	00101111	INCHES		01011111	WEIGHT		10001111		

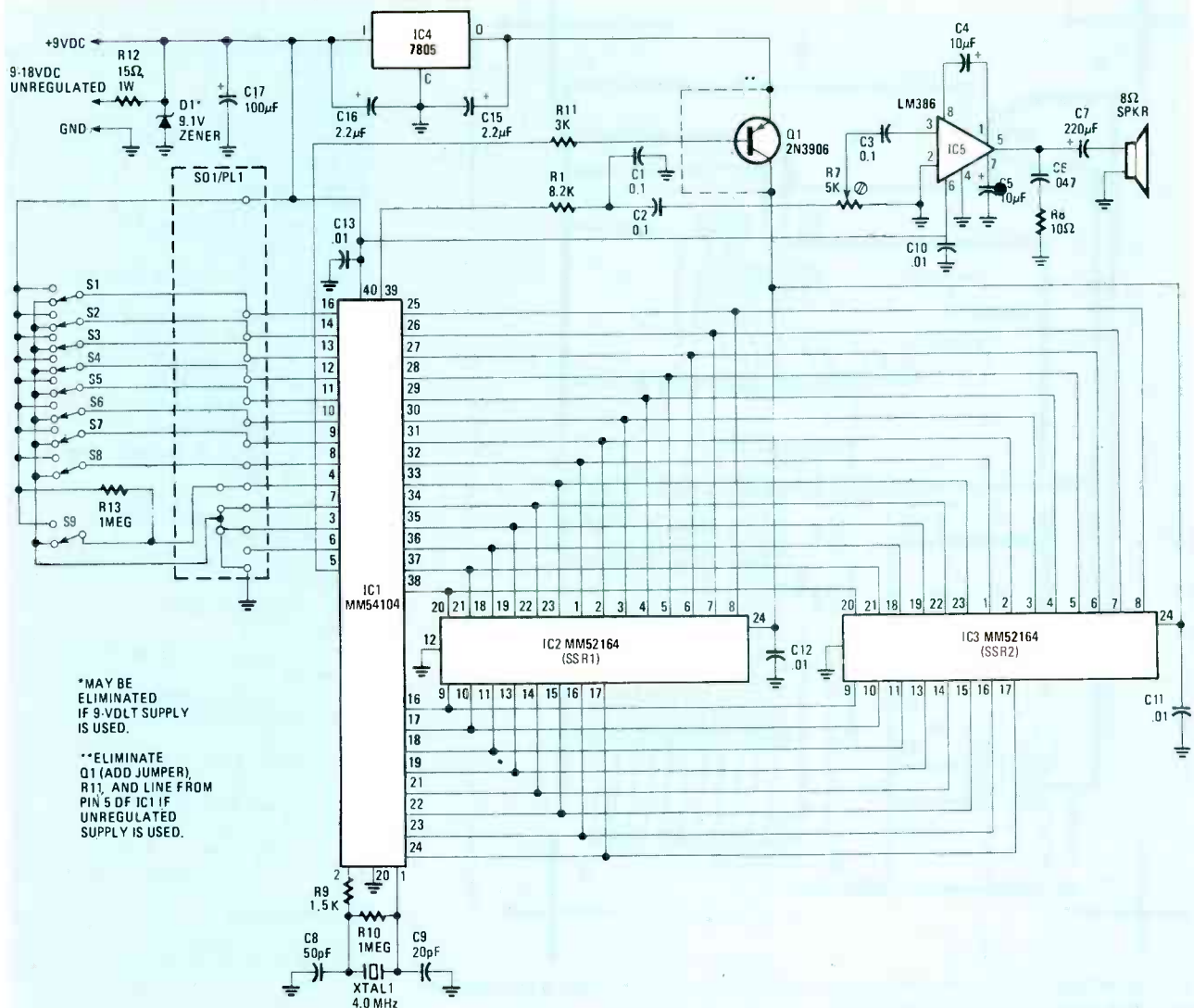


FIG. 3—SPEECH SYNTHESIZER can be operated from either a 9-volt battery or an unregulated DC-supply. See text for more details.

sion-techniques is a system capable of storing and reconstructing a word or phrase with high quality.

### How it works

The complete speech-synthesizer circuit consists of the speech processor IC (SPC), plus the speech ROM's, power supply, filter, and audio amplifier. The speech data is mask-programmed into the ROM's by National Semiconductor, starting from an ordinary analog tape containing the words and phrases required.

The speech waveforms are time-domain compressed, eliminating a great deal of the number-crunching required by other techniques to reconstruct the digitized word. Because of that, the SPC can operate at lower clock-frequencies, and the speech-reconstruction circuit becomes simpler to build. Inside the SPC there is a programmable frequency-generator and a variable-gain D/A converter. Together, they produce the intonation and inflection

that make for realistic-sounding speech.

The ROM set specified in the Parts List is programmed with a vocabulary (see Table 1) consisting of 136 words, one complete phrase, two tones, and five different silence durations. The words are in a male voice and the phrase is in a female voice. Each word or phrase to be synthesized is assigned an 8-bit address. Address 81H (the "H" indicates that the number is hexadecimal) is the "ss" hissing sound; it is used after a word to make it plural. All addresses higher than 8FH are invalid and will result in garbled sounds.

The circuit, shown in Fig. 3, is quite simple to build. It can be powered either by a 9-volt transistor battery connected to the REGULATED DC input or from 9 to 18-volts DC applied to UNREGULATED input. Resistor R12 and Zener diode D1 are used to obtain 9-volts if an unregulated source is used; they may be omitted if a 9-volt battery is used. The 9-volts is used by the SPC and the audio amplifier.

Power for the ROM's (5-volts) is derived from the 9-volt supply by IC4, a 7805 5-volt regulator. That power can be switched on or off by the SPC's ROMEN line using resistor R11 and transistor Q1, a useful feature for extending battery life. If an unregulated supply derived from a transformer is used you can omit R11 and Q1 and add a jumper between the pads for what would have been Q1's collector and emitter.

A clock network—resistors R9 and R10, capacitors C8 and C9, and XTAL1—is used with active components inside the SPC IC form a 4-MHz clock. The remaining circuits are the filter and audio amplifier.

The filter is a simple passive R-C circuit whose component values are chosen for a 200-Hz rolloff frequency. The output of the filter is supplied to a voltage divider, which acts as a volume control. The signal is then amplified by IC5, which drives a 8-ohm speaker. (Use a fairly large speaker—small 2 1/4-



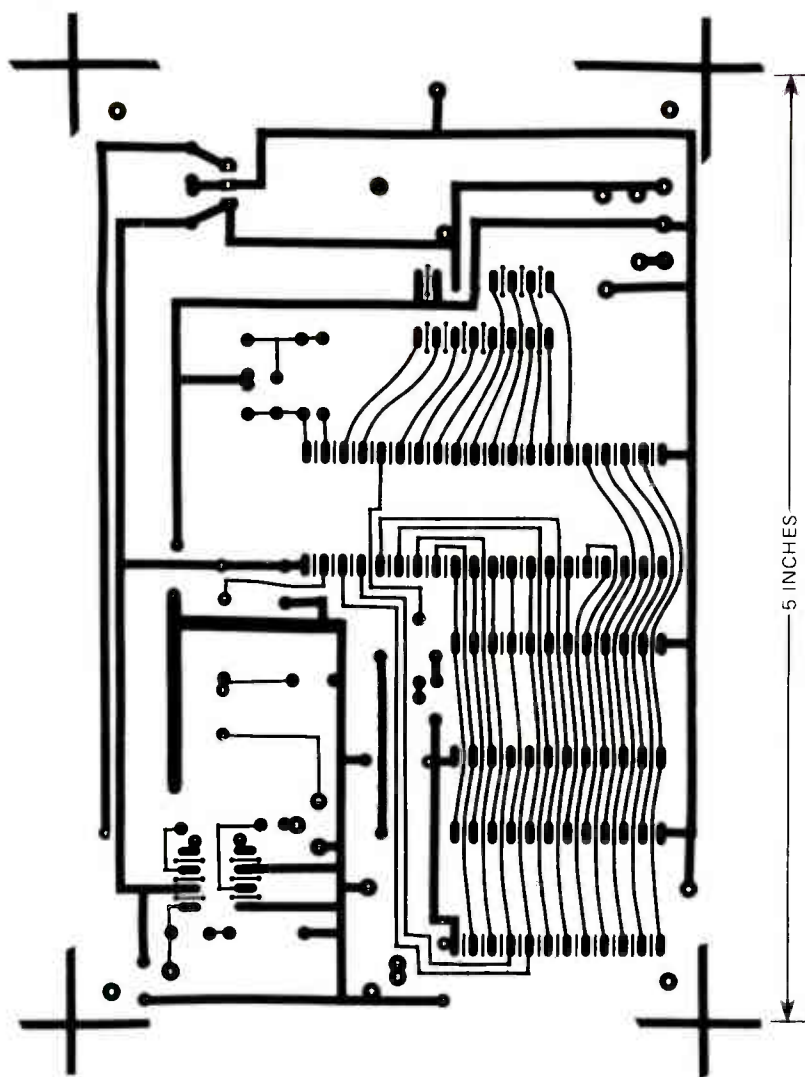


FIG. 4—SYNTHESIZER IS CONSTRUCTED on single-sided PC board. You may wish to eliminate feed-through traces between IC pins to prevent shorts.

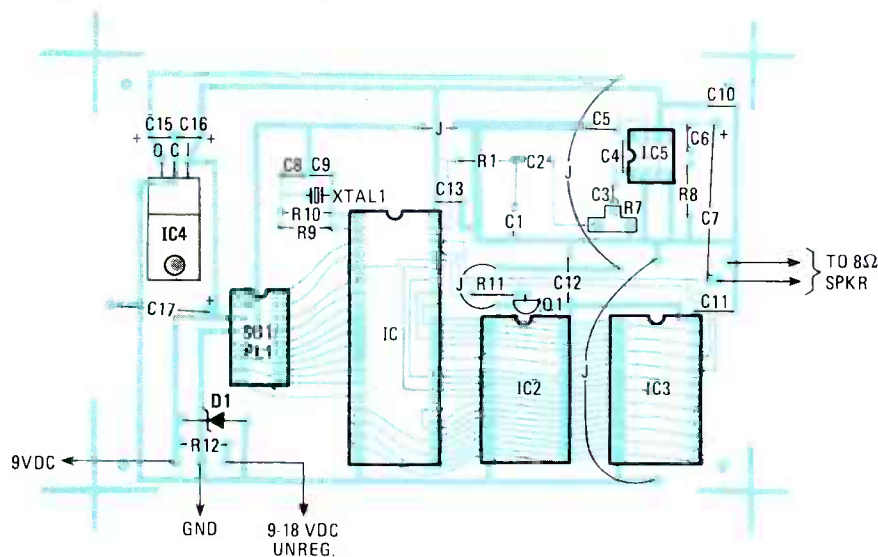


FIG. 5—PARTS-PLACEMENT DIAGRAM shows board with components for both 9-volt battery and unregulated-DC operation. Refer to text for information on which parts can be eliminated.

inch ones tend to distort the sound.)

### Construction

A foil pattern for the circuit board is provided in Fig. 4. An already etched-

and-drilled board is also available; see the Parts List. Install the IC sockets, together with the jumpers required for your configuration, as shown in Fig. 5. Then install and solder the resistors,

### PARTS LIST

All resistors 1/4 watt, 5% unless otherwise noted

R1—8200 ohms  
R2-R6—not used  
R7—5000 ohms, PC-mount trimmer potentiometer  
R8—10 ohms  
R9—1500 ohms  
R10, R13—1 megohm  
R11—3000 ohms  
R12—15 ohms, 1 watt (see text)

#### Capacitors

C1-C3—0.1  $\mu$ F, ceramic disc  
C4, C5—10  $\mu$ F, tantalum  
C6—0.047  $\mu$ F, ceramic disc  
C7—220  $\mu$ F, electrolytic  
C8—50 pF, ceramic disc  
C9—20 pF, ceramic disc  
C10-C13—0.01  $\mu$ F, ceramic disc  
C14—not used  
C15, C16—2.2  $\mu$ F, tantalum  
C17—100  $\mu$ F, electrolytic

#### Semiconductors

IC1—MM54104 speech processor IC (National)  
IC2—MM52164 SSR1 speech ROM (National)  
IC3—MM52164 SSR2 speech ROM (National)  
IC4—7805 5-volt regulator  
IC5—LM386 audio amp  
Q1—2N3906  
D1—9.1-volt Zener  
XTAL1—4.0 MHz crystal  
SO1—16-pin DIP socket  
PL1—16-pin DIP header  
S1-S8—SPDT slide or toggle switch  
S9—SPDT momentary slide or toggle switch

**Miscellaneous:** PC board, switch-mounting board, 8-ohm speaker, IC sockets, 9-volt battery, or 9-18-volt DC power supply, etc.

The following are available from Quest-Star Electronics, 2820 Howard Dr., Las Vegas, NV 89107: IC1-IC3, \$105.00; PC board, \$12.95; kit of all parts, \$149.95. Add \$1.75 for shipping and handling; NV residents please add tax. Allow 6-8 weeks for delivery. For information on other speech-ROM sets, send an SASE to Quest-Star Electronics.

capacitors, and crystal. Finally, install the diode, transistor, and IC4. You are now ready to test the synthesizer.

Before inserting the rest of the IC's in their sockets, apply power to the board. The sockets for IC1 and IC5 should have 9-volts at their  $V_{CC}$  pins (pins 40 and 6, respectively). Pin 3 of IC4—its output—should read 5 volts. If you used Q1, pin 24 ( $V_{CC}$ ) of IC2 and IC3 will be at ground potential. If you ground pin 5 of the SPC (IC1) socket, 5-volts should appear on pin 24 of the two IC's. If everything checks out, disconnect power and discharge the filter capacitors.

Connect the speaker and install all the IC's in their sockets. Connect the switches as shown in the schematic

*continued on page 110*

OF THE EIGHT MAJOR  
CAPACITANCE INSTRUMENTS  
MADE, ONLY THE CM-100...

# DETECTS LEAKAGE

(and at half the price!)

**\$89<sup>95</sup>**



**Usefulness** — Measure capacitors 10pF — 500μF; leakage 1 nA or .005 C.V., whichever is greater. **Accuracy** — To 2% depending on range. **Dependability** — Ruggedized construction; 1 yr. warranty. **Versatility** — In circuit measurement of capacitance and leakage. Output signal proportionate to measurement. **Portability** — 350 Hr. Battery Life.

\*To 25,000μF with external voltmeter


Send check, address (NO P.O. BOX) plus \$3.50 Handling. CT res. add 7½% tax.

Phone orders: (203) 423-7940

**ANDERS PRECISION INSTRUMENT CO., INC.**  
4 Bridge St. Plaza, P. O. Box 75 Willimantic, CT 06226

CIRCLE 41 ON FREE INFORMATION CARD
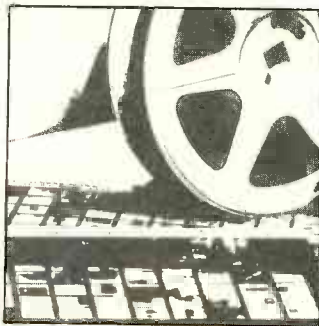
## This Publication is available in Microform.



**University Microfilms  
International**


Please send additional information

for \_\_\_\_\_  
Name \_\_\_\_\_  
Institution \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

300 North Zeeb Road  
Dept. P.R.  
Ann Arbor, MI. 48106


## SPEECH SYNTHESIZER

continued from page 46

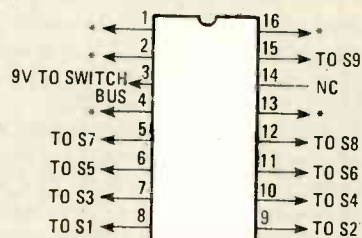

PINS MARKED WITH "\*" CONNECT  
TO SWITCH GROUND BUS.

**FIG. 6—CONNECTIONS FROM PL1.** This same arrangement can be used for connection to a computer's parallel port.

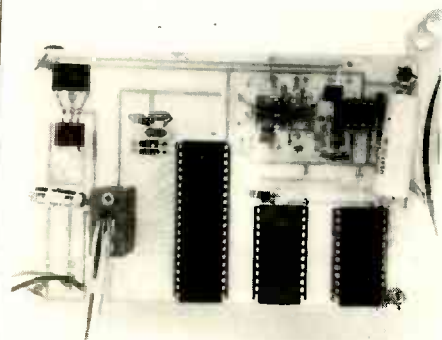

**FIG. 7—PROTOTYPE OF the speech synthesizer.** DIP header at top of board is not used in version described here.

(Fig. 3) and Fig. 6, using a DIP header for PL1 to mate with SO1 on the board. The completed board is shown in Fig. 7.

Apply power to the circuit and set S1 through S8 in the logic-zero (grounded) position. Now throw switch S9. You should hear a female voice say, "This is *Digitalker*."

Set switch S1 in the logic-one (9-volts) position, throw S9 and you will hear in a male voice say, "One." As you increment the switch address in binary fashion and throw S9 each time, the count will continue, "...two, three, four," etc. Table 1 shows the contents of each binary address; using that table to set the switches, you'll be able to put the synthesizer through its paces.

After you've had enough of throwing switches, you can unplug them and connect the board to your computer via a parallel port. Now, with a simple program your computer will be able to say things like, "TIME IS UP. PLEASE TRY AGAIN." You will quickly learn how to combine *pieces* of the pre-programmed words to form new words, as well; since output stops each time you access the SPC, it is a simple matter to slice phonemes out of several words and recombine them.

R-E

## Radio-Electronics REPRINT BOOKSTORE

- |  |               |  |               |
|--|---------------|--|---------------|
| <input type="checkbox"/> Build Your Own Satellite TV Receiver .....    | \$7.00        | <input type="checkbox"/> Radio-Electronics back issues (1980) .....    | (each) \$3.50 |
| <input type="checkbox"/> 8-Ball Satellite TV Antenna .....             | \$5.00        | (March, May 1980 not available)  |               |
| <input type="checkbox"/> Build Your Own Robot .....                    | \$12.00       | Write in issues desired _____  |               |
| <input type="checkbox"/> TV Descrambler (January, February 1981) ..... | \$3.00        | <input type="checkbox"/> Radio-Electronics back issues (1978-79) ..... | (each) \$4.00 |
| <input type="checkbox"/> Video Entertainment (January 1982) .....      | \$2.00        | (October, November 1978 not available)                                 |               |
| <input type="checkbox"/> Your Own Computer (October 1981) .....        | \$3.00        | Write in issues desired _____  |               |
| <input type="checkbox"/> Radio-Electronics Back issues (1981) .....    | (each) \$3.00 | <input type="checkbox"/> Special Projects (Spring 1981) .....          | \$4.00        |
| (February, March, December 1981 not available)                         |               | <input type="checkbox"/> How To Make PC Boards .....                   | \$2.00        |
| Write in issues desired _____  |               | <input type="checkbox"/> All About Kits .....                          | \$2.00        |

To order any of the items indicated above, check off the ones you want. Complete the order form below, include your payment—check or money order (DO NOT SEND CASH), and mail to Radio-Electronics, Reprint Department, 200 Park Ave. South, New York, NY 10003. Please allow 4 - 6 weeks for delivery.

If you need a copy of an article that is in an issue we indicate is unavailable you can order it directly from us. We charge 50¢ per page. Indicate the issue (month & year) pages and article desired. Include payment in full, plus shipping and handling charge.

### MAIL TO:

Radio-Electronics  
Reprint Department, 200 Park Ave. South, New York, NY 10003

All payments must be in U.S. funds

Total price of order .....

Sales Tax (New York State Residents only) .....

Shipping & Handling (U.S. & Canada only) .....

(includes FIRST CLASS POSTAGE)

\$1.00 per item .....

All Others (\$2.00 per item, sea mail) .....

(\$4.00 per item, air mail) .....

Total Enclosed .....

Name .....

Address .....

City .....

State .....

Zip .....